

Use of Simulated Annealing in Quantum Circuit Synthesis

Manoj Rajagopalan
17 Jun 2002

Outline

- **Overview**
- Simulated Annealing: the idea used
- Implementation
- Results
- Conclusions and Future Work

Quantum Circuit Synthesis

- Input-output transformation specified
- Objective: Gates and their arrangement into a circuit to achieve this transformation
- Methods:
 - Factorization <vshende> (Cybenko)
 - Enumeration <gmathew, akprasad> (exhaustive, B&B)
 - Genetic Algorithms <smaddipa> (Williams+, Yabuki+)
 - Simulated Annealing <rmanoj> ()

Synthesis by SA

- Choose whole circuit every time
- Use equivalent transformations (optimization)
- Incremental modification (ends of circuit)
 - Computationally efficient!
 - But is it good enough?
- Hey, what is Simulated Annealing?

Optimization Problems

- State variables:
 - Reflect the system state
 - May not be directly modified
- Control variables (degrees of freedom):
 - Affect the state
 - Directly modified
- Constraints on state and control (equality/inequality)
- Objective: Solve for optimum of scalar objective function

Optimization Heuristics

- Search space is too large for exhaustive enumeration, too complex to visualize
- Pick random solutions and evaluate performance index (PI)
- Filter good/best solution(s)
- Perturb these and re-evaluate PI
- Incorporate means to avoid local minima

Simulated Annealing: Basic Idea

- Objective: minimize scalar function subject to given constraints
- Select one initial solution and evaluate cost
- Perturb the solution and calculate new cost
- Improvement in cost?
 - Yes: Copy perturbed solution to initial solution
 - No: Probabilistically accept perturbed solution (to avoid local minima)

Quantum Circuit Synthesis as an Optimization Problem

- Select type, number and location of gates (control)
- Evaluate equivalent unitary operator (state)
- Constraint: Operator == given unitary
- Objective: Minimize number of gates


Outline

- Overview
- **Simulated Annealing: the idea used**
 - Incremental perturbation
- Implementation
- Results
- Conclusions and Future Work

SA: Quantum Circuit Synthesis


- Assume given operator can be synthesized
- Number of qubits known for given operator
- Choose entire circuits in each perturbation?
 - How many gates?
 - What location?
 - Need to 'multiply' all gates to get equivalent operator each time!
- Alternative: Incremental modification (at ends of circuit each time): NOP, ADD, REM, REP
- Qubits handled independently

SA: Incremental Perturbation

 

ADD: Hadamard Gate to #1

SA: Incremental Perturbation

 


ADD: Hadamard Gate to #1

SA: Incremental Perturbation

- Equivalent Operator =


$$\begin{pmatrix} I \\ \otimes \\ H \\ \otimes \\ I \\ \otimes \\ I \end{pmatrix} \times \left[\begin{array}{c} \text{Original} \\ \text{Operator} \end{array} \right]$$

SA: Incremental Perturbation

 

REMove: Hadamard Gate from #0

SA: Incremental Perturbation

 


REMove: Hadamard Gate from #0

SA: Incremental Perturbation

- Equivalent Operator =


$$\left[\begin{array}{c} \text{Original} \\ \text{Operator} \end{array} \right] \times \begin{pmatrix} H \\ \otimes \\ I \\ \otimes \\ I \\ \otimes \\ I \end{pmatrix}$$

SA: Incremental Perturbation

 

REPlace: T Gate on #2 with X Gate

SA: Incremental Perturbation

 


REPlace: T Gate on #2 with X Gate

SA: Incremental Perturbation

- Equivalent Operator =


$$\left[\text{Original} \quad \text{Operator} \right] \times \begin{pmatrix} I \\ \otimes \\ I \\ \otimes \\ T^\dagger \\ \otimes \\ I \end{pmatrix} \times \begin{pmatrix} I \\ \otimes \\ I \\ \otimes \\ X \\ \otimes \\ I \end{pmatrix}$$

SA: Incremental Perturbation

 


REPlace: CNOT on #1-3 with CNOT on #3-2

SA: Incremental Perturbation

 

REPlace: CNOT on #1-3 with CNOT on #3-2

SA: Incremental Perturbation

 

REPlace: CNOT on #1-3 with CNOT on #3-2

SA: Incremental Perturbation

- Equivalent Operator =

$$\begin{pmatrix} I \\ \otimes \\ C \\ \otimes \\ NOT \\ \otimes \\ I \end{pmatrix}
 \begin{pmatrix} I \\ \otimes \\ H \\ \otimes \\ I \\ \otimes \\ I \end{pmatrix}
 \begin{pmatrix} I \\ \otimes \\ I \\ \otimes \\ NOT \\ \otimes \\ C \end{pmatrix}
 \begin{pmatrix} I \\ \otimes \\ C^\dagger \\ \otimes \\ I \\ \otimes \\ NOT^\dagger \end{pmatrix}
 \begin{pmatrix} I \\ \otimes \\ H^\dagger \\ \otimes \\ I \\ \otimes \\ I \end{pmatrix}
 \begin{pmatrix} I \\ \otimes \\ C^\dagger \\ \otimes \\ NOT^\dagger \\ \otimes \\ I \end{pmatrix}
 \begin{pmatrix} I \\ \otimes \\ I \\ \otimes \\ I \\ \otimes \\ I \end{pmatrix}
 \left[\begin{matrix} \\ \\ \\ \\ \\ \\ \\ \end{matrix} \right]
 \begin{matrix} \\ \\ \\ \\ \\ \\ \\ \end{matrix}
 \left[\begin{matrix} \\ \\ \\ \\ \\ \\ \\ \end{matrix} \right]$$

Outline

- Overview
- Simulated Annealing: the idea used
- **Implementation**
 - Data Structures
 - Algorithm
 - Annealer Configuration
 - Hardware and Software Platforms
- Results
- Conclusions and Future Work

Data Structures

- Class *qgate*: Quantum gates & operators
- Qubit: *list<qgate>*
- Circuit: Array of qubits
- *qgate* instance for CNOTs duplicated on control and target qubits

SA Algorithm

- Initial circuit = empty
- Initial operator = I
- For each qubit
 - For head and tail of qubit, each
 - Choose one out of 4 moves: NOP, ADD, REM, REP in a non-conflicting manner.
 - Choose gates required for these, if applicable
- Evaluate new operator, guarding special cases
- Calculate (frobenius) norm of deviation from given unitary

SA Algorithm

- Out of a few (10) such moves, choose move with minimum deviation norm
- Is this below tolerance (10^{-6}) ?
 - Yes: Synthesis complete! Return.
 - No: Is this 'cost' better than that previously accepted?
 - Yes: Accept this move into circuit
 - No: Accept this move with probability $e^{(-\Delta \text{cost} / T)}$

SA Algorithm

- Repeat this procedure for a few (10) trials.
- Change temperature according to schedule.
- Iterate whole procedure till temperature lower limit is reached.

Annealer Configuration

- Moves:
 - 4 equiprobable changes at each end of qubit: NOP, ADD, REM, REP
- 1 or 10 moves per trial
- 1 or 10 trials per iteration
- 1001 iterations:
 - Tstart = 1
 - Tend = 0.001
 - Temperature schedule = linear with step 0.001
- Objective: Simply minimize deviation norm (no circuit size reduction yet) (tolerance = 10^{-6})

Platforms


- proton.eecs.umich.edu
- AMD Athlon @ 1194 MHz 256kB cache
- Debian linux (kernel v2.4.18)
- Coded in C++
- g++ 2.95.4 with `-O3` optimization
- Timing and peak memory tracking using `getrusage()`

Outline

- Overview
- Simulated Annealing: the idea used
- Implementation
- **Results**
 - Single qubit circuits
 - Circuits with CNOT gates
- Conclusions and Future Work

Results: simple {H,X,Z} circuits

 - TEST I
 - Randomly generated, 3 qubits, 30 gates
 - Optimal equivalent:



Results(1/2): TEST I

	Using {H, X, Z}		Using {H, X}	
	# gates	Time(s)	# gates	Time(s)
Min	4	0	6	0.09
Max	22	1.57	72	1.95
Avg	9	0.33	26	0.76
	97% success rate		61% success rate	

Results(2/2): TEST I

	Using {H, Z}		Using {H, X, S}	
	# gates	Time(s)	# gates	Time(s)
Min	6	0	5	0.11
Max	47	1.84	23	1.71
Avg	10	0.35	12	0.66
	17% success rate		54% success rate	

Results: Simple {H, X, Z} circuits

- TEST II
 - Randomly generated
 - 5 qubits, 300 gates

Results(1/3): TEST II

	Using {H, X, Z}		Using {H, X, S}	
	# gates	Time(s)	# gates	Time(s)
Min	6	0.02	7	0.06
Max	74	3.54	127	15.11
Avg	17	0.60	27	5.53
	100% success rate		82% success rate	

Results(2/3): TEST II

	Using {H, Z}		Using {H, X}	
	# gates	Time(s)	# gates	Time(s)
Min	8	0.06	10	0.05
Max	58	11.54	178	13.98
Avg	23	1.82	52	3.48
	99% success rate		81% success rate	

Results(3/3): TEST II


	Using {H, S}		Using {H, T}	
	# gates	Time(s)	# gates	Time(s)
Min	12	0.46	28	19.86
Max	94	17.71	28	19.86
Avg	29	4.23	28	19.86
	81% success rate		1 % success rate	

{H, X, Z}: Conclusions

- Easily synthesized
- Optimal equivalents detected
- Average number of gates is impressive!
- Versatility of annealer: wide variety of gate libraries
- Fast!

Results: Circuits with CNOTs

 - Brassard's teleportation circuit
 - Careful with the gates (especially S and T) !



Results(1/3): Send Circuit

	Using {L, CNOT, R}		Using {CNOT, H, S _{NC} }	
	# gates	Time(s)	# gates	Time(s)
Min	4	0	21	1.1
Max	213	99.68	199	84.17
Avg	53	11.23	70	23.17
	95 % success rate		8 % success rate	

Results (2/3): Send Circuit

	Using {CNOT, H, X}		Using {CNOT, H, Z}	
	# gates	Time(s)	# gates	Time(s)
Min	20	0.75	8	0.06
Max	301	100.38	357	107.00
Avg	125	31.43	162	38.46
	51 % success rate		45 % success rate	

Results(3/3): Send Circuit

	Using {CNOT, H, X, S _{NC} , T _{NC} }		Using {R, S, T, L, X, CNOT}	
	# gates	Time(s)	# gates	Time(s)
Min	-	-		
Max	-	-		
Avg	-	-		
	0 % success rate		? % success rate	

Send Circuit: Conclusions

- Difficult to synthesize with overspecified gate library
- Using 10 trials per iteration instead of the usual 1 improves chances of getting an equivalent circuit and may even detect optimal one but takes much more time and may show worse average performance

Results(1/2): Receiver Circuit

	Using {S, CNOT, T}		Using {CNOT, H, S _{NC} }	
	# gates	Time(s)	# gates	Time(s)
Min	4	0	4	0
Max	20	0.52	16	0.72
Avg	5	0.05	6	0.11
	100 % success rate 83% find optimum		100 % success rate 68% find optimum	

Results(2/2): Receiver Circuit

	Using {S _{NC} , CNOT, T _{NC} , X, H}		Using {R, S, T, L, X, CNOT}	
	# gates	Time(s)	# gates	Time(s)
Min	3	0		
Max	16	1.19		
Avg	5	0.22		
	100 % success rate 44% find optimum		? % success rate ? % find optimum	

Receiver Circuit: Conclusions

- A lot easier to synthesize than the send circuit
- Variety of gate libraries can be used
- Overspecified gate library not a problem
- Annealer finds optimum quite often.

Teleportation circuit: Previous Work

- Williams and Gray
 - Objective: minimize discrepancy, sum of absolute value of matrix of differences
 - Send and receive minimal circuits have 4 gates each. Achieved. 3 using N&C gates
- Yabuki and Iba
 - Receive circuit needs minimum of 3 gates. We get 4 using given library and 3 using N&C gates

Outline

- Overview
- Simulated Annealing: the idea used
- Implementation
- Results
- **Conclusions and Future Work**

Overall Conclusions

- Annealer is versatile over a range of discrete gate sets using a very simple configuration
- Incremental perturbation works very well (Igor rules!)

Future Work

- Optimizations
 - Compose single qubit gates into one operator
- Ideas
 - Optimal synthesis: include # gates in PI
 - Circuits equivalent upto a nonzero global phase
 - Annealer configurations (types and probabilities of moves, temperature schedule) based on plots of quality of solution against iterations
 - More challenging problems: Toffoli gates (increased interqubit interaction) , single qubit rotations (continuous values)