

Fault Testing for Reversible Circuits

Ketan Patel

November 6, 2002

Outline

- Motivation
- Reversible Circuits
- Fault Models
- Test Set Constructions (Upper Bounds)
- Integer Linear Programming Formulation
- Future Work

Motivation

Reversible Circuits

- “Energy-free” computation
- Reversible applications: **cryptology, DSP, etc.**
- Important class of quantum circuits

Efficient testing will be important


Reversible Gates (Examples)

NOT Gate




Input	Output
0	1
1	0

C-NOT Gate

 


Input	Output
00	00
01	01
10	11
11	10

TOFFOLI Gate

 


Input	Output
000	000
001	001
010	010
011	011
100	100
101	101
110	111
111	110

Sample Circuit

 

Notation & Terminology

 - n # of inputs/outputs
- l # of gates
- k_i size of i th gate
- d circuit depth
- f_j function of first j levels
- f_j^{-1} inverse function




Properties of Reversible Circuits

Controllability: Wires at any level can be set to any state


Observability: Any change in intermediate state changes output

Fault Models

Stuck-at Model: Wire stuck at 0 (or 1)

 


Cell Fault Model: Single component fails

 

Goal

Generate (minimal) set of input vectors which can detect any fault in F

Example:

 


Use vector **0100** to detect fault

Goal

Generate (minimal) set of input vectors which can detect any fault in F

Example:

 

Use vector **0100** to detect fault

Correct output: **0010**

Faulty output: **1110**

Test set is **complete** if it detects all faults in set

General Conditions

Stuck-at Fault Model:

Test set is complete \Leftrightarrow every fault site can be set to both 0 and 1

$$\# \text{ of faults} = 2 \cdot \left(n + \sum_{i=1}^l k_i \right)$$

Cell Fault Model:

Test set is complete \Leftrightarrow all input patterns occur at input of every gate

$$\# \text{ of faults} = \sum_{i=1}^l 2^{k_i}$$

Here we focus on stuck-at model


Basic Upper Bounds

$$|T| \leq 2^{n-1} + 1$$

Each fault site set to 0 (or 1) by half input vectors

$$|T| \leq d + 1$$
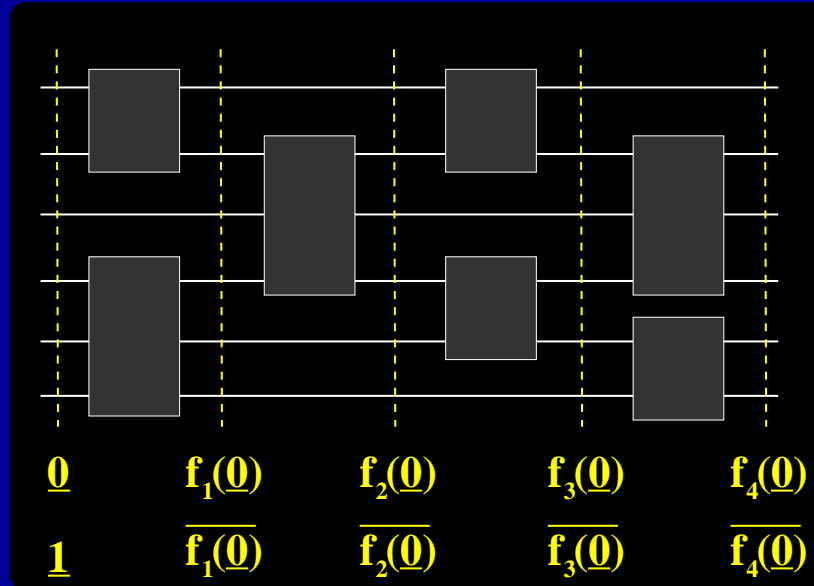
$$\{\underline{0}, \underline{1}, f_1^{-1}(\overline{f_1(\underline{0})}), \dots, f_d^{-1}(\overline{f_d(\underline{0})})\}$$



Efficient Test Sets Exist

Lemma If test set covers C faults

$\Rightarrow \exists$ input vector covering $\geq \frac{1}{2}$ remaining faults.

Corollary

$$|T| \leq \left\lceil \log_2 \left(n + \sum_{i=1}^l k_i \right) \right\rceil + 2$$

\Rightarrow Efficient test set exists

Example: if $n = 64$, $l = 10^6$, and $k_i = 3$ then $|T| \leq 23$

...but proof “non-constructive”

Integer Linear Programming Formulation

- t_i decision variable representing
input vector i
- T_i n -bit expansion of int i
- $f_j(T_i)$ values at level j for input T_i

Minimize $t_0 + t_1 + \dots + t_{2^n-1}$

subject to the constraints

$$\sum_i f_j(T_i) \cdot t_i \geq \underline{1}$$

$$\sum_i \overline{f_j(T_i)} \cdot t_i \geq \underline{1}, \quad 0 \leq j \leq d$$

where $t_i \in \{0, 1\}$, $0 \leq i \leq 2^n - 1$

2^n variables and $2n(d+1)$ constraints \Rightarrow infeasible for large circuits

C-NOT Example

Minimize $t_0 + t_1 + t_2 + t_3$
subject to the constraints

$$a) \quad t_0 + t_1 \geq 1 \quad t_2 + t_3 \geq 1$$


$$b) \quad t_0 + t_2 \geq 1 \quad t_1 + t_3 \geq 1$$

$$c) \quad t_0 + t_1 \geq 1 \quad t_2 + t_3 \geq 1$$

$$d) \quad t_0 + t_3 \geq 1 \quad t_1 + t_2 \geq 1$$

where $t_0, t_1, t_2, t_3 \in \{0, 1\}$


⇒ need 3 test vectors

 

Circuit Decomposition

Alternate approach:

 - decompose circuit into shorter subcircuits acting on fewer wires
- iteratively apply ILP method
- dynamically combine test sets




Circuit Decomposition

Solving ILP for C_0 gives

x_0	x_1	x_2	x_3	x_4	x_5
X	0	1	X	1	1
X	1	0	X	0	0
X	1	1	X	1	0

Passing these through C_0 gives

x_0	x_1	x_2	x_3	x_4	x_5
X	1	1	X	0	0
X	1	0	X	1	0
X	0	0	X	1	1

 

Circuit Decomposition

Generate ILP for C_1 & add constraints

$$\begin{array}{c|c} x_0 & x_1 & x_4 & x_5 \\ \hline X & 1 & 0 & 0 \\ X & 1 & 1 & 0 \\ X & 0 & 1 & 1 \end{array} \in T \Rightarrow \begin{array}{c|c} \text{Constraints} \\ \hline t_4 + t_{12} \geq 1 \\ t_6 + t_{14} \geq 1 \\ t_3 + t_{11} \geq 1 \end{array}$$


Yields solution $t_6 = t_{11} = t_{12} = 1$

New test set

x_0	x_1	x_2	x_3	x_4	x_5
1	1	1	X	0	0
0	1	0	X	1	0
1	0	0	X	1	1

Passing through C_1 gives

x_0	x_1	x_2	x_3	x_4	x_5
0	1	1	X	0	0
1	1	0	X	1	0
1	0	0	X	1	1

 

Circuit Decomposition


Generate ILP for C_2 & add constraints

x_0	x_1	x_4	x_5	$\in T \Rightarrow$	Constraints
0	1	1	X		$t_6 + t_7 \geq 1$
1	1	0	X		$t_{12} + t_{13} \geq 1$
1	0	0	X		$t_8 + t_9 \geq 1$

Yields solutions $t_5 = t_7 = t_8 = t_{12} = 1$

New test set

x_0	x_1	x_2	x_3	x_4	x_5
0	1	1	1	0	0
1	1	0	0	1	0
1	0	0	0	1	1
0	1	0	1	X	X

 

Test Set Compaction


Test sets via decomposition method may be redundant

Find smallest subset of complete vectors: **compaction**


Use ILP method with subset of t_i 's

Much easier to solve than overall ILP if original test set small

Simulation Results

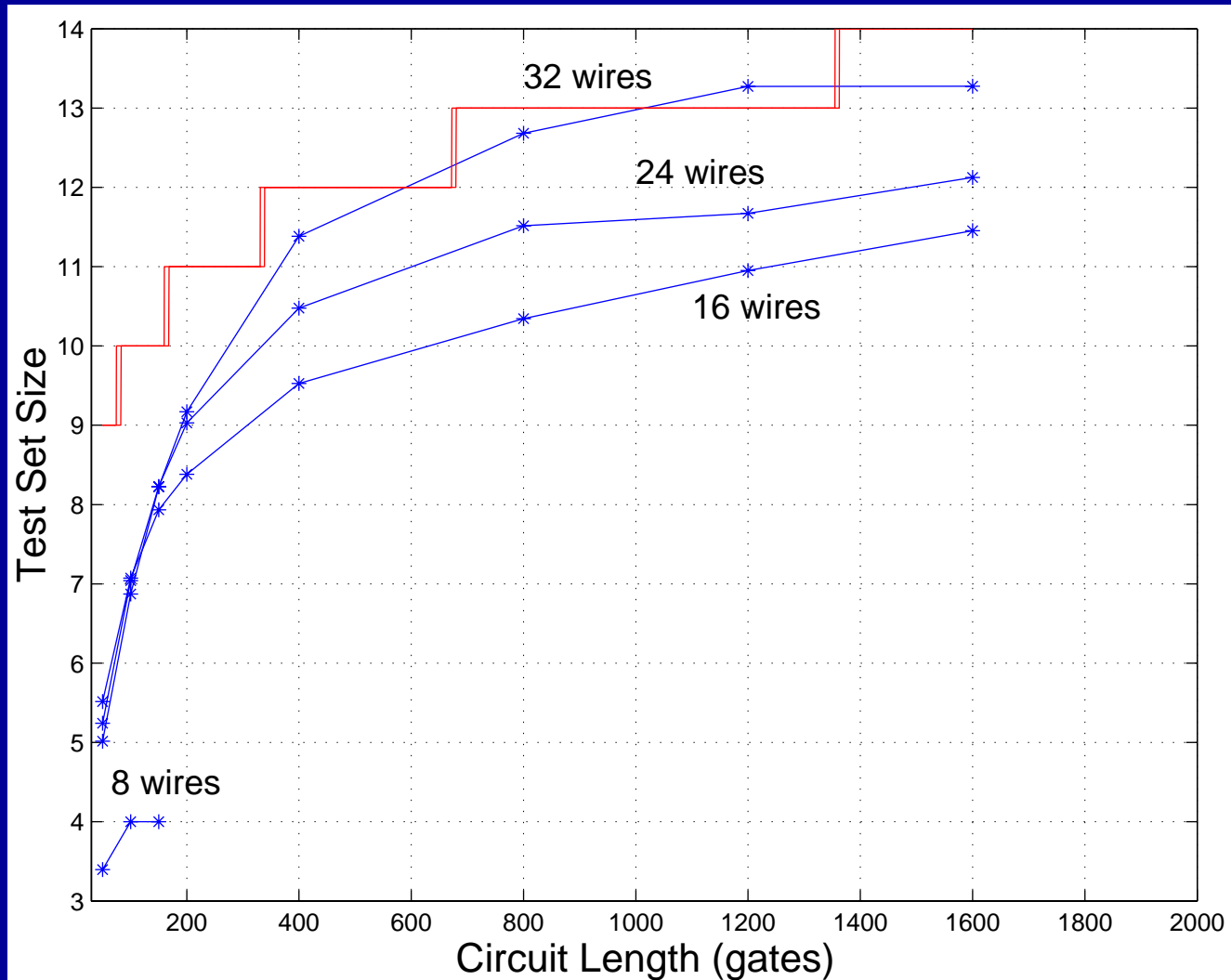

Simulation Results (Compaction)

 

Cell Fault Model

$$|T| \leq 2^n - 2^{n-k_1} + 1$$

$$|T| \leq \left(\sum_{i=1}^l 2^{k_i} \right) - l + 1$$

$$|T| \leq \sum_{i=1}^l \left\lceil \frac{2^{k_i}}{i} \right\rceil$$

where circuit has l gates w/ sizes $k_1 \geq k_2 \geq \dots k_l$

ILP and decomposition methods work as in stuck-at case

Future Work

- Lower Bounds
- Circuits with Known Minimal Test Sets
- Connections with Circuit Synthesis
- Fault Diagnosis
- Quantum Circuits